



Circuit Analysis Fundamentals

Basic Circuit Elements

Resistor (R)	Opposition to current flow. Measured in Ohms (Ω). Ohm's Law: $V = IR$
Capacitor (C)	Stores electrical energy. Measured in Farads (F). $I = C(dV/dt)$
Inductor (L)	Stores energy in a magnetic field. Measured in Henries (H). $V = L(dI/dt)$
Voltage Source (V)	Provides a constant voltage. Ideal voltage source has zero internal resistance.
Current Source (I)	Provides a constant current. Ideal current source has infinite internal resistance.

Circuit Laws

Kirchhoff's Current Law (KCL)	The algebraic sum of currents entering a node is zero. $\sum I = 0$
Kirchhoff's Voltage Law (KVL)	The algebraic sum of voltages around a closed loop is zero. $\sum V = 0$
Ohm's Law	Relates voltage, current, and resistance: $V = IR$
Power (P)	Rate at which energy is transferred. $P = VI = I^2R = V^2/R$
Series Resistors	Equivalent resistance: $R_{eq} = R_1 + R_2 + \dots + R_n$
Parallel Resistors	Equivalent resistance: $1/R_{eq} = 1/R_1 + 1/R_2 + \dots + 1/R_n$

Circuit Analysis Techniques

Nodal Analysis: Solve for node voltages using KCL. Choose a reference node (ground).
Mesh Analysis: Solve for loop currents using KVL. Suitable for planar circuits.
Superposition Theorem: Find the response due to each independent source acting alone, then sum the individual responses. Only applicable for linear circuits.
Thevenin's Theorem: Replace a complex circuit with a voltage source (V_{th}) in series with a resistor (R_{th}).
Norton's Theorem: Replace a complex circuit with a current source (I_n) in parallel with a resistor (R_n). $R_n = R_{th}$

Electromagnetics

Fundamental Constants

Permittivity of Free Space (ϵ_0)	$\epsilon_0 \approx 8.854 \times 10^{-12}$ F/m
Permeability of Free Space (μ_0)	$\mu_0 = 4\pi \times 10^{-7}$ H/m
Speed of Light (c)	$c \approx 3 \times 10^8$ m/s

Magnetostatics

Magnetic Field (B)	Measured in Tesla (T) or Webers per square meter (Wb/m ²)
Magnetic Force (F)	On a moving charge: $F = q(v \times B)$
Ampère's Law	Relates magnetic field to current: $\oint B \cdot dl = \mu_0 I_{enc}$
Inductance (L)	Ability of a conductor to store energy in a magnetic field: $L = \Phi/I$ (Henries)

Electromagnetic Waves

Maxwell's Equations (Differential Form):
$\nabla \cdot D = \rho$
$\nabla \cdot B = 0$
$\nabla \times E = -\partial B/\partial t$
$\nabla \times H = J + \partial D/\partial t$
Poynting Vector (S): Represents the power flow of an electromagnetic wave. $S = E \times H$ (W/m ²)
Wave Impedance (η): Ratio of electric field to magnetic field in a medium. $\eta = \sqrt{\mu/\epsilon}$

Electrostatics

Electric Field (E)	Force per unit charge. $E = F/q$ (N/C or V/m)
Electric Potential (V)	Potential energy per unit charge. $V = U/q$ (Volts)
Coulomb's Law	Force between two point charges: $F = k * (q_1 q_2) / r^2$, where $k = 1 / (4\pi\epsilon_0)$
Capacitance (C)	Charge stored per unit voltage: $C = Q/V$ (Farads)

Digital Logic

Basic Logic Gates

AND Gate	Output is 1 only if all inputs are 1.
OR Gate	Output is 1 if at least one input is 1.
NOT Gate	Inverts the input. If input is 1, output is 0, and vice versa.
NAND Gate	NOT + AND. Output is 0 only if all inputs are 1.
NOR Gate	NOT + OR. Output is 1 only if all inputs are 0.
XOR Gate	Exclusive OR. Output is 1 if inputs are different.

Boolean Algebra

Basic Theorems:
$A + 0 = A$
$A + 1 = 1$
$A \cdot 0 = 0$
$A \cdot 1 = A$
$A + A = A$
$A \cdot A = A$
Commutative Laws:
$A + B = B + A$
$A \cdot B = B \cdot A$
Associative Laws:
$(A + B) + C = A + (B + C)$
$(A \cdot B) \cdot C = A \cdot (B \cdot C)$
Distributive Laws:
$A \cdot (B + C) = A \cdot B + A \cdot C$
$A + (B \cdot C) = (A + B) \cdot (A + C)$
DeMorgan's Theorems:
$(A + B)' = A' \cdot B'$
$(A \cdot B)' = A' + B'$

Power Systems

AC Power Fundamentals

RMS Voltage (V_{rms})	Root Mean Square voltage. $V_{rms} = \frac{V_{peak}}{\sqrt{2}}$ (for sinusoidal waveforms)
RMS Current (I_{rms})	Root Mean Square current. $I_{rms} = \frac{I_{peak}}{\sqrt{2}}$ (for sinusoidal waveforms)
Apparent Power (S)	$S = VI^*$ (VA)
Real Power (P)	$P = VI \cos(\theta)$ (Watts)
Reactive Power (Q)	$Q = VI \sin(\theta)$ (VARs)
Power Factor (PF)	$PF = \cos(\theta) = P / S $

Transformers

Turns Ratio (a): $a = N_p / N_s = V_p / V_s = I_s / I_p$
N_p, N_s : Number of turns in primary and secondary windings.
V_p, V_s : Voltage in primary and secondary windings.
I_p, I_s : Current in primary and secondary windings.
Ideal Transformer Equation: $V_p \cdot I_p = V_s \cdot I_s$

Combinational Logic Circuits

Multiplexers (MUX): Select one of several input signals and forward it to the output.
Demultiplexers (DEMUX): Direct a single input signal to one of several outputs.
Encoders: Convert a set of inputs into a binary code.
Decoders: Convert a binary code into a set of outputs.
Adders: Perform binary addition (Half Adder, Full Adder).

Sequential Logic Circuits

Flip-Flops: Basic memory elements (SR, D, JK, T).
Registers: Groups of flip-flops used to store binary information.
Counters: Sequential circuits that count pulses (Asynchronous, Synchronous).

Three-Phase Power

Line Voltage (V_L)	Voltage between two lines in a three-phase system.
Phase Voltage (V_{ph})	Voltage across a single phase.
Line Current (I_L)	Current flowing through a line in a three-phase system.
Phase Current (I_{ph})	Current flowing through a single phase.
Y-Connection	$V_L = \sqrt{3} \cdot V_{ph}$, $I_L = I_{ph}$
Delta-Connection	$V_L = V_{ph}$, $I_L = \sqrt{3} \cdot I_{ph}$
Three-Phase Power (P)	$P = \sqrt{3} \cdot V_L \cdot I_L \cdot \cos(\theta)$

Power System Protection

Fuses: Overcurrent protection. Melt and interrupt the circuit.
Circuit Breakers: Overcurrent protection. Can be reset after tripping.
Relays: Detect abnormal conditions and initiate protective actions.
Grounding: Provides a low-impedance path for fault currents.